


Midterm Exam 2

Exam duration: 1.5 hours, 4 questions


1.

a. What is the effective width and length of the combination


i. Asdf

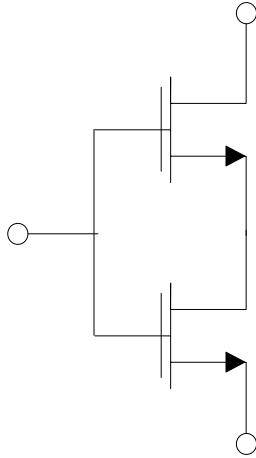


ii.

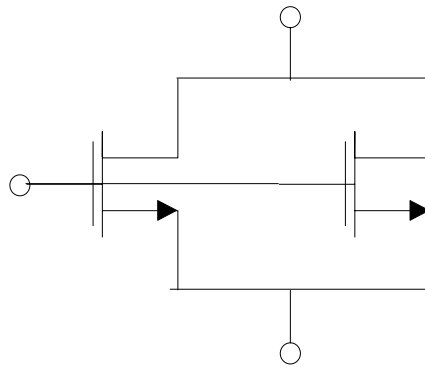

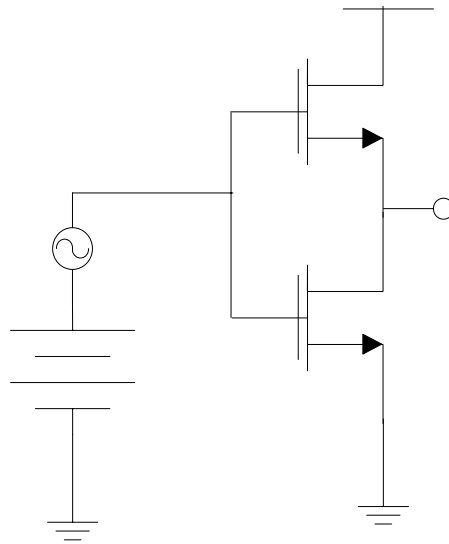
- b. What is the small signal low frequency gain V_{out}/V_{in} ? (Ignore all capacitances. M1 and M2 in saturation. Answer in terms of small signal parameters).



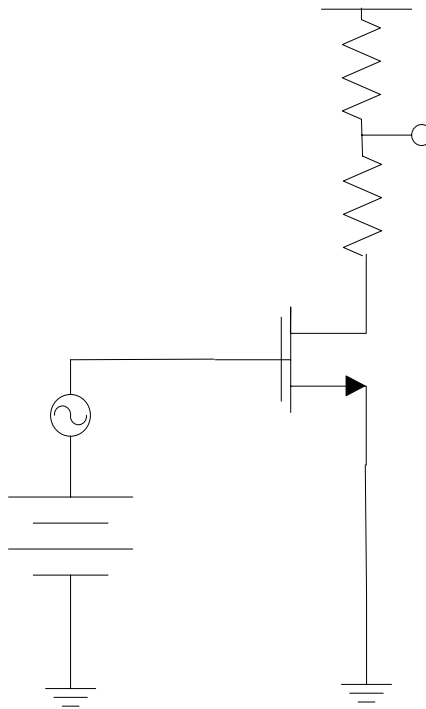
- c. Assume M1 in saturation, $\lambda=0$, ignore all capacitances.
- Draw the small signal model
 - What is the small signal low frequency gain?



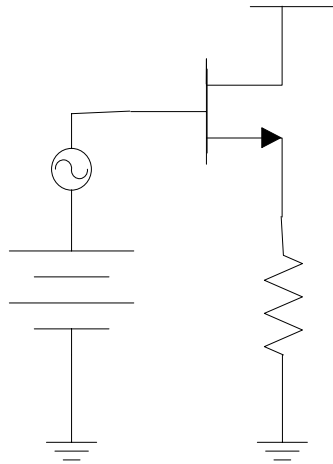
- d. Assume source and bulk are connected, $\lambda=0$, ignore all capacitances. M1 is a PMOS transistor and is in saturation.
- Draw the arrow that indicates the source terminal
 - Write an expression for the small signal low frequency gain = V_{out}/V_{in}



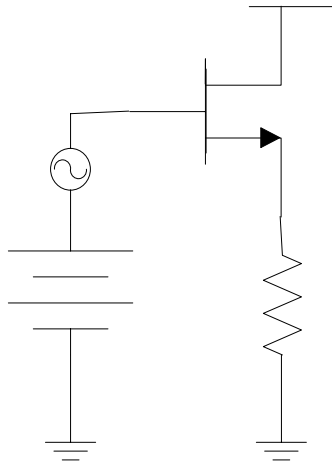
- e. Assume source and bulk are connected, $\lambda=0$, ignore all capacitances. M2 is an NMOS transistor and is in saturation.
- Draw the arrow that indicates the source terminal
 - Write an expression for the small signal low frequency gain = V_{out}/V_{in}



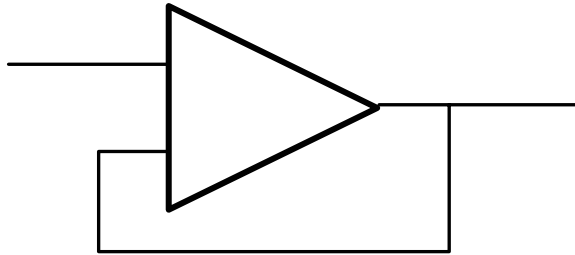- f. What is the feedback factor, β ?
- i.



- ii.

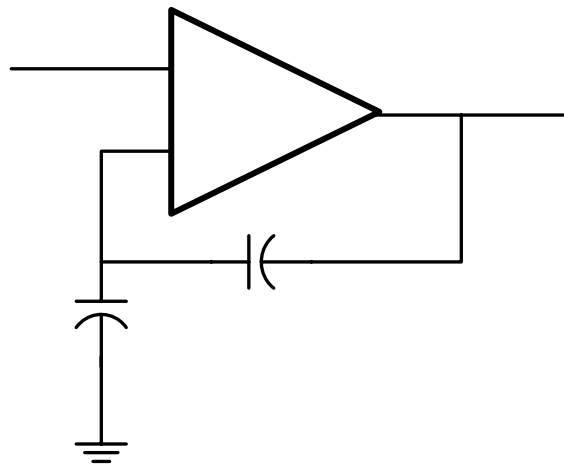


- g. An amplifier with a gain of 1000 and an output resistance of $10\text{k}\Omega$ is connected in unity gain feedback. What is the output resistance of the overall circuit.
- h. If the amplifier from part g. has a single pole at 100kHz , then what is the -3dB frequency of the entire circuit?


2.

- a. An amplifier connected in unity gain feedback has a phase margin of 30 degrees. What is the gain of the overall system at the amplifier's unity gain frequency?
- b. The amplifier from a. has two poles, ω_{p1} , ω_{p2} and no zeros. Assume that $|\omega_{p2}| \gg |\omega_{p1}|$. What is the relationship between $|\omega_{p2}|$ and the unity gain frequency of the amplifier?
- c. Sketch a bode plot showing the gain of the amplifier and the gain of the overall system versus frequency.
- d. If the amplifier has only a single pole $|\omega_{p1}|$ and it is much less than the unity gain frequency, then what is the phase margin?

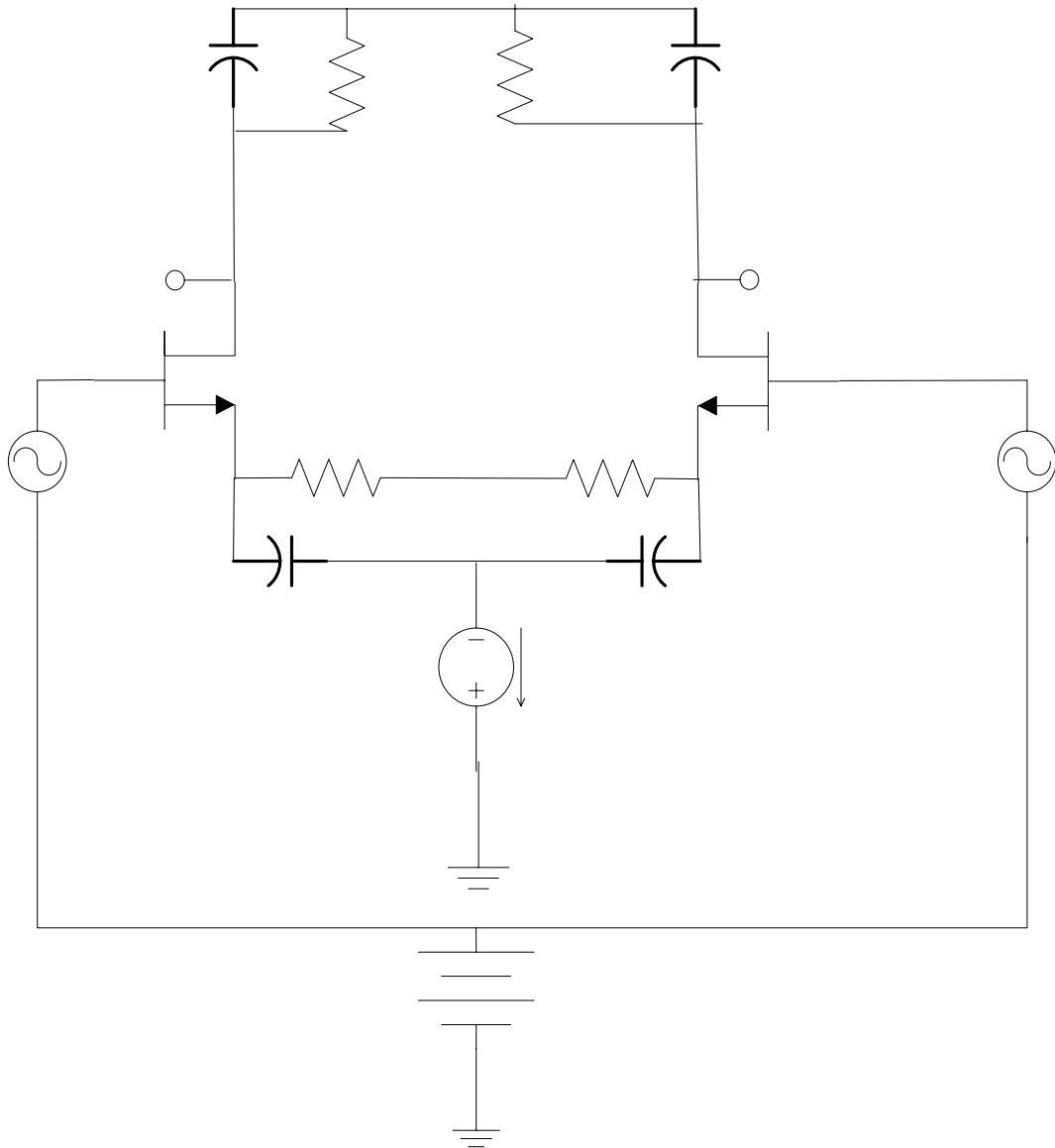3. Assume that $M1=M2$ and both are in saturation. Ignore body effect and assume that $\lambda=0$. Ignore all capacitances except those shown (C_L and C_S). $V_{out}=V_{out+} - V_{out-}$
- Using symmetry or otherwise, derive an expression for the small signal low frequency gain V_{out}/V_{in} .
 - Derive an expression for the frequency dependent gain $V_{out}/V_{in}(s)$.
 - Identify the poles and zeros
 - Sketch the Bode and Phase plots. Assume that $R_S C_S < R_L C_L$
 - Explain what is happening at the different regions in the Bode plot



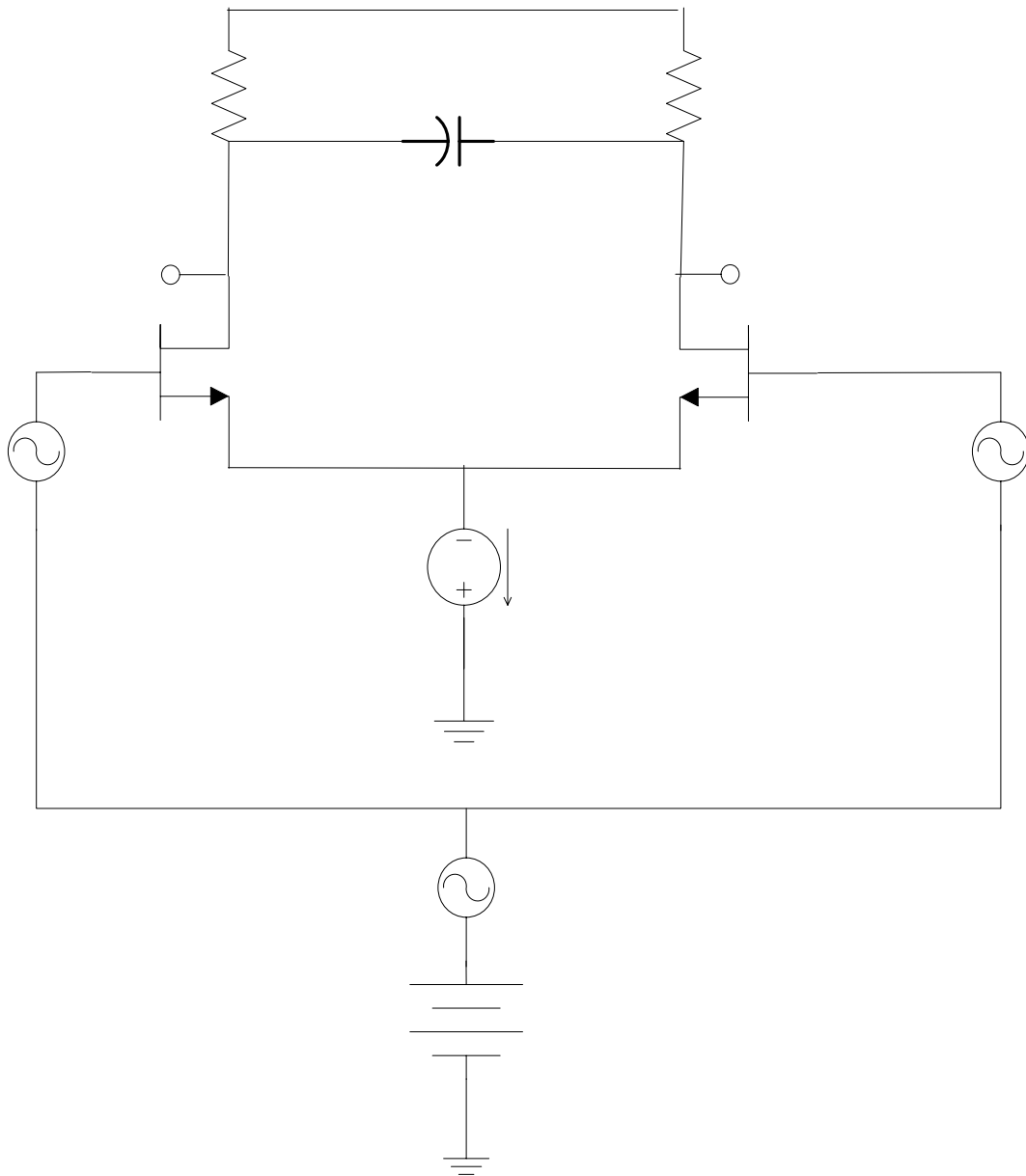4. Assume that $M1=M2$ and both are in saturation. Ignore body effect and assume that $\lambda=0$. Ignore all capacitances except those shown (C_L and C_S). $V_{out}=V_{out+} - V_{out-}$
- Write an expression for the frequency dependent gain V_{out}/V_{in} (s). (i.e A_{DM}).
 - Write an expression for the common mode gain V_{out}/V_{in} (s). (i.e A_{CM}). Recall: $V_{out+}/V_{CM}(s)=V_{out-}/V_{CM}(s)$.



5. Assume that $M1=M2$ and both are in saturation. Ignore body effect and assume that $\lambda=0$. Ignore all capacitances except those shown (C_L and C_S). $V_{out}=V_{out+} - V_{out-}$
- Write an expression for the frequency dependent differential gain $V_{out}/V_{in}(s)$. (i.e $A_{DM}(s)$).
 - Write an expression for the frequency dependent common mode gain $V_{out}/V_{in}(s)$. (i.e A_{CM}).
 - Sketch the Bode showing A_{CM} , A_{DM} versus frequency. Assume that $R_S C_S < R_L C_L$

